

notes.txt

#### Flip-flop:

- Setup time: minimum time from when input D is stable to rising clock edge
  - input must propagate through internal gates
- Hold time: minimum time for D to remain stable after rising clock edge
  - input must propagate through internal feedback gates

#### D latch:

- sets memory by input whenever clock is high
- (not on rising edge of clock)

#### D flop flop

- sets value on rising clock edge
  - and thus, only once per clock cycle
- internally it is two d-latches chained together:
  - the first with an inverter in front of it's clock
  - the second without
- value of D is available at Q immediately after rising clock edge

#### T flip flop

- on rising edge of clock toggles state if T (input) is high
- if T is low, keeps current value
- IS edge triggered

#### shift register

- called n-bit shift register
  - n is how many bits it stores
- accepts one bit a a time as input
  - (this is serial)
- outputs all bits at the same time, one pin for each bit
- also has a out pin for chaining multiple together
- internally it is a chain of flip flops
  - previous output goes to next input, so the data shifts down the line

#### rotate register

- a shift register with it's output connected to it's input
- rotates the stuff in it's buffer

#### universal shift register

- shift register with lots of other functions
- e.g. clear, clock, shift, right, left, load, read, control

#### shifter

- just a different combination of wires that moves the bits over
- can be designed to map one of the edge bits to the filler bits

#### barrel shifter

- shifter that can shift any arbitrary number of bits
- barrel shifter with n shifters can shift between 0 and  $(2^n - 1)$  bits
- e.g. 3 shifters goes 0-7

- and uses shifters of 1, 2, and 4 bits

#### fraction multiplication approximation in binary

- compute  $A/3$ , error  $\leq 5$ 
  - each numerator is picked using:
    - \*  $\text{numerator} = (2^{\hat{x}} / \text{desired\_divisor})$
  - $1/3 = 1/4$ , error:  $(0.25 - 1/3) = 0.08 \rightarrow 25$
  - $1/3 = 3/8$ , error:  $(0.375 - 1/3) = 0.04 \rightarrow 12.5$
  - $1/3 = 5/16$ , error:  $(0.3125 - 1/3) = 0.02 \rightarrow 6$
  - $1/3 = 11/32$ , error:  $(0.34375 - 1/3) = 0.01 \rightarrow 3$
- 11/32:
  - $(8+2+1)/32$
  - $(2^{\hat{3}} + 2^{\hat{1}} + 2^{\hat{0}})/2^{\hat{5}}$
  - $A/3 = (C_{ii3} + (C_{ii1}) + (C_{ii0}))_{ii5}$

#### counter

- n-bit counter has n bits
  - one design uses n-bit increment-er and n-bit register
- designed to roll over, so that you can chain multiple together
  - has an 'overflow' bit for that reason
  - overflow is bitwise AND of all output bit numbers
    - \* (AND is highest representable number)
  - must have a count pin separate from clock pin
    - \* so that they can be on the same clock when chained
- down-counter counts down instead of up
  - it's overflow is bitwise NAND of all register bits
- limit a counter to any arbitrary value:
  - make circuit that matches that binary value (outputs 1 only when it gets that value)
  - wire the output of that circuit to the reset pin of the counter

#### bidirectional counter

- must have different carry bit
- when counting down, you want NOR all inputs as carry (matches 0)

#### parallel vs serial

- parallel
  - n-bits wide
  - n bits move every clock cycle
  - the bus is n wires plus the clock
  - usually slower clock than serial
- serial
  - one bit wide
  - one bit moves every clock cycle
- you can convert serial data to parallel using a shift register and clock divider

#### serial addition

- add a number bit by bit
- you store the sum in a shift register because that can accept serial input
- slower than parallel adder, but uses far fewer gates

#### register file

- pins: clock, w\_data, w\_addr, w\_en, r\_data, r\_addr, r\_en
- more than one register in one chip
- writing
  - w\_data is wired to all registers
    - \* (buffers are used to make sure the signal doesn't get weak from length)
  - w\_addr and w\_en go to a decoder which enables one of the registers
- reading
  - the output of every register is wired to the data in port of a driver
  - r\_addr is wired to a decoder
  - the output of that decoder is wired to the enable port of each driver
  - the output of every driver is directly connected to r\_data
  - this is safe because the decoder ensures that only one of the drivers is ever active

#### clock divider:

- used to take a fast clock input and output a slower output
- use a count up counter
- if it's a power of 2, you can use an n-bit counter and tc (clock overflow) as clock output
- if it's not a power of 2:
  - up counter
    - \* add logic to reset the counter when it reaches the desired number of ticks
    - \* connect divided clock output to that reset
  - down counter
    - \* set the load input to the desired number of ticks (as constant inputs)
    - \* wire reset to load
    - \* connect divided clock output to that reset
- the pulse width of the clock output may be different than you expect
  - it will be right for the power of 2 case
  - but for the other case, it is probably wrong
- there will be a phase difference that is very difficult to fix
  - due to gate delay

#### clock timing:

- to find maximum clock speed, use the formula:
  - $T = (\text{clk-}\lambda Q) + (\text{max } Q\text{-}\lambda D) + \text{setup time} + \text{skew}$
  - \* T clock period

- $1/T = \text{clock frequency}$
- \*  $\text{clk-}\lambda Q$ : delay of one flip-flop
  - interval of time after clock rising edge where Q has correct value
- \*  $\text{max } Q\text{-}\lambda D$ : most delayed path from ANY flip-flop output to ANY flip-flop input
  - the input/output don't have to be on the same flip-flop
- \* setup time:
  - length of time after the clock rising edge that D must remain the same value in order for the flip-flop to function
- \* skew: optional, clock skew of the circuit
  - (if not given, it is 0)

#### metastability

- happens when
  - you have asynchronous input (e.g. human pres-able button)
  - you break the setup time or hold time
- when output is metastable it is somewhere between 0 and 1
  - you can't predict where it is
- fix for button:
  - wire it into a synchronizer flip-flop and then to the rest of your circuit
    - \* (because flip-flop uses the same clock as the rest of your circuit)
  - maybe more than one synchronizer flip-flop for a very clean signal
    - \* (at the expense of one clock cycle delay each)

#### glitching

- outputs that are initially not stable
  - e.g. signal flip flops a little before settling on the correct value
- happens because not all inputs get to the logic at the same time due to gate delay and stuff
- fix by putting a d-latch or flip-flop after the output
  - called registered output
  - this way the output isn't seen until the next clock cycle
  - (the output is assumed to be stable by then. If it isn't, you probably need a longer clock cycle)
  - you can combine that flip flop into the state register

#### FSM: Finite State Machine

- usually store the state in a state register
  - could also use a collection of flip flops, shift register or whatever
- to prove that two edges are disjunct:
  - AND together the boolean expressions, and simplify
  - you should end up at 0 because it is never possible to satisfy both transitions
- to prove that one condition is always satisfiable
  - OR together all boolean expressions and simplify

- \* you should get true because one of them is true for every input
- normal state encoding
  - assign a number to each state
  - use the binary representation of that number
  - allows for the smallest register possible
- one-hot encoding
  - for n states, use a n-bit register
  - each state is n binary bits with one 1 and the rest 0
  - may allow for simpler next-state logic

#### FSM state reduction

- group states of FSM by what they output
- then, for each input:
  - sub-group the groups by next state according to every combination of that input
- after all this, if 2 states are always in the same group, they are duplicates

#### FSM -> circuit: (will be on final)

- 1. assign each state a value for the state register to hold
  - don't worry about optimizations yet
- 2. make truth table
  - inputs: current state, inputs to FSM
  - outputs: next state, output
- 3. design circuit using truth table
  - current state + inputs -> next state logic
- if you're asked to match a bit pattern, it is easier to use a shift register
- (or make one out of d-flip-flops)

#### FSM reducing states:

- group by z-value
- sub-group by arrows pointing into them
- and then by arrows pointing out
- then any states in the same group are duplicates

#### Mealy vs Moore FSM:

- Moore
  - output is dependent on current state only
    - \* when input changes, output does not change until next clock cycle
  - output logic can be separated completely from next state logic
    - \* (output logic is then not dependent on inputs)
- Mealy
  - outputs on arrows
  - output is dependent on state and inputs
    - \* when input changes, output changes asynchronously
    - \* (potentially not to the correct value)
  - means outputs are not lined up with clock edges
  - Mealy and Moore FSMs can be combined

#### HLFSM: High Level Finite State Machine

- compared to normal FSM:
  - multi-bit input/output
  - local storage
  - arithmetic operations
    - \* (FSM can only do boolean, since everything is 1 bit anyway)
  - a state transition can be a more complex expression
    - \* e.g. (in\_reg < 5)
- convention:
  - := for assignment
  - == for equality comparison
  - '0' for single bit value
  - 0 for integer value
  - "00" for multi-byte value
    - \* multi-byte outputs must be local storage

#### RTL Design: Register Transfer Level Design

- high-level description of the logic involved
- uses multi-byte I/O and generic blocks
  - multi-byte I/O is like arrays
- like a block diagram
  - too complex for a normal FSM, so design with a HLFSM

#### RAM memory types

- register file
  - discussed previously
- SRAM: Static RAM: Random Access Memory
  - uses 2 inverters back-to-back
- DRAM: Dynamic RAM
  - uses special on-chip capacitors to store data
  - data is encoded in the charge of the capacitor, so it is possible to store multiple bits per cell
  - requires special chip design, so it's usually a separate chip as everything else
  - charge value can decay, so it must be refreshed
    - \* (usually taken care of by the chip firmware)
- size:
  - register file: lots of transistors/cell (least dense)
  - SRAM: 6 transistors/cell
  - DRAM: 1 transistor/cell (most dense)
- Speed:
  - register file: fastest
  - SRAM
  - DRAM: slowest
- RAM has setup/hold times just like flip-flops

## ROM: Read Only Memory

- non-volatile
- can be very fast
- low power
- does not need to be refreshed (like DRAM)
- PROM: Programmable Read Only Memory
  - can be written to only once
  - implemented using fuses or ant-fuses
- EPROM: Erasable Programmable Read Only Memory
  - written to using higher-than-normal voltage
  - erased by exposure to UV light
    - \* meaning chip must have a window
- EEPROM: Electrically Erasable Programmable Read Only Memory
  - EPROM than can be erased electrically

## MEMS: Micro Electrical Mechanical System

- tiny chip-sized devices that aren't necessarily gates or stuff
- e.g. gyroscopes

## Queue

- FIFO: First in, First Out
- visualize as a circle
- contains limited max size elements
- 2 pointers: front and rear
- push (write):
  - write to address rear
  - increment rear
- pop (read):
  - read from address front
  - increment front
  - does not really destroy content, it is still accessible
- if front or rear reaches size:
  - next value should be 0
- if rear == front:
  - could mean full or empty
  - depends if this happens after read or write
  - after write: it's full
  - after read: it's empty

### making a FSM for a Queue is a good exercise

- should probably do this as studying for the exam

## RTL tradeoffs

- Latency
  - time from data input to data output in seconds
- Throughput

- how many jobs can you input per second
- pipelining
  - do things in stages, like an assembly line
  - helps with throughput
  - does not help with latency
  - put a pipeline register in in-between steps
  - doesn't make task faster, but you can start a new task before the previous one finishes
- concurrency:
  - do things side by side
  - helps with throughput but not latency
- it is sometimes possible to do both concurrency and pipelining
- component allocation:
  - choice of components used to implement design
  - example: if you have 2 states that need multiplication:
    - \* it might be more compact to have them use the same multiplier and simply MUX the inputs
    - \* slightly more delay, many fewer gates
- operator binding:
  - how you configure the MUXes in compact allocation
  - if you map them efficiently you can reduce delay
  - e.g. if one input is used in more than one scenario, arrange the inputs such that that one always has the same port
    - \* and then, you don't need a MUX there at all
- operator scheduling:
  - introduce new states to preform operations
    - \* downside is more states
    - \* upside is states do fewer things each
      - \* (which means fewer gates)
  - e.g. to reduce the number of multipliers required
  - can reduce the longest path through the circuit which allows you to increase the clock speed
- other optimizations:
  - serial vs concurrent computation
    - \* datapath: carry-ripple (serial) vs carry-lookahead adder (parallel)

## chip design types

- full custom
  - exactly what it sounds like, gate for gate design
  - very hard to make
  - takes a long time from design to mass production
  - cheapest per chip in large quantities
  - most expensive per chip if you're making only one
    - \* (very much in the realm of "Why would you do that!?!")
- standard cell ASIC: Application Specific Integrated Circuit

- has pre laid out cells
- each cell can be made into a gate
- you must still make custom mats to fabricate the circuit
- vs full custom
  - \* easier
  - \* bigger and slower
  - \* more expensive per chip
- gate array
  - structured ASIC
  - gates are already on the chip, they just need to be wired together
  - vs standard cell ASIC
    - \* faster and easier to manufacture
    - \* bigger and slower
    - \* more expensive per chip
  - some use only NAND or NOR gates
    - \* since both of those are Turing complete
- FPGA: Field Programmable Gate Array
  - like a gate array that you can reprogram on the fly
    - \* at least the original ones were.
    - \* modern ones use lookup tables
  - vs gate array
    - \* easier
    - \* slower
    - \* more expensive
    - \* bigger
      - no non-recurring costs
- Single IC's
  - like the stuff we did in the first few labs
  - does not scale at all
- SPLD: Single Programmable Logic Device
  - predates FPGAs
  - prefabricated IC with large AND and OR structure
  - has programmable nodes before each AND gate
    - \* could be fuse based (not reusable)
    - \* or memory based (reusable)
  - used to implement simple logic

how a FPGA works

- ### TODO
- LUT = Look Up Table
  - MUX + memory
  - example: 3 binary inputs = 8 combinations
  - use 8-1 MUX map 8 pre-computed input values
  - if a circuit uses more inputs than a LUT can handle, you must cascade to more than one LUT

- \* (just like you do with gates)
  - \* this is more efficient than larger memories anyway
  - it is common for a LUT to have fewer than it's maximum inputs
    - \* thus the extra data is wasted, but that isn't a big deal
  - you can also have LUTs with more than one bit outputs
  - SM: Switch Matrices
    - AKA programmable interconnect
    - the way that LUTs are connected together
    - also MUX+memory based
    - each output is MUXed to an input
  - CLB: Configurable Logic Block
    - LUT + flip-flop + MUX + memory
    - memory programs MUX to output stored (flip flop) value or logic value
  - chip layout
    - hundreds of thousands of SMs and CLBs in a grid with wires connecting adjacent blocks
- programming a FPGA
- all memory of all blocks is connected sequentially as one big shift register
    - known as a scan chain
  - you shift in your configuration (code) that does stuff and then the FPGA is programmed

### TODO: processor internals