

**Metric Prefixes**

peta	P	$10^{15}$	1 000 000 000 000 000
tera	T	$10^{12}$	1 000 000 000 000
giga	G	$10^9$	1 000 000 000
mega	M	$10^6$	1 000 000
kilo	k	$10^3$	1 000
hecto	h	$10^2$	100
deca	da	$10^1$	10
one		$10^0$	1
deci	d	$10^{-1}$	0.1
centi	c	$10^{-2}$	0.01
milli	m	$10^{-3}$	0.001
micro	$\mu$	$10^{-6}$	0.000 001
nano	n	$10^{-9}$	0.000 000 001
pico	p	$10^{-12}$	0.000 000 000 001
femto	f	$10^{-15}$	0.000 000 000 000 001

**Ohm's Law**  $V = IR$ ,  $I = \frac{V}{R}$ ,  $R = \frac{V}{I}$

**Battery Symbol**

The side with the longer line is the positive side

**Complex Numbers**

- $z = x + iy = re^{i\theta} = r[\cos(\theta) + i\sin(\theta)]$
- $[r(\cos(\theta) + i\sin(\theta))]^n = r^n[\cos(n\theta) + i\sin(n\theta)]$
- $z^n = (re^{i\theta})^n = r^n e^{in\theta}$
- $\frac{1}{i} = -i$
- $\sqrt[n]{z} = \sqrt[n]{r} e^{i\frac{\theta}{n} + \frac{2k\pi}{n}}$  for  $n \in \mathbb{N}^*$  (ints  $\geq 0$ )
- $e^{j\theta} = \cos(\theta) + j\sin(\theta) \quad \left| \quad e^{-j\theta} = \cos(\theta) - j\sin(\theta) \right.$
- $\cos(\theta) = \frac{1}{2}(e^{j\theta} + e^{-j\theta}) \quad \left| \quad \sin(\theta) = \frac{1}{2j}(e^{j\theta} - e^{-j\theta}) \right.$
- normalized:  $\text{sinc}(t) = \frac{\sin(\pi t)}{\pi t}$
- $\left| \frac{a}{b} \right| = \frac{|a|}{|b|} \quad \angle \frac{a}{b} = \angle a - \angle b$

**Trig**

$$\begin{aligned} \cos(2a) &= \cos^2(a) - \sin^2(a) = 2\cos^2(a) - 1 = 1 - 2\sin^2(a) \\ \cos^2(a) + \sin^2(a) &= 1 \quad \left| \quad \sin(2a) = 2\sin(a)\cos(a) \right. \\ \cos^2(a) &= \frac{1}{2}(1 + \cos(2a)) \quad \left| \quad \sin^2(a) = \frac{1}{2}(1 - \cos(2a)) \right. \end{aligned}$$

**Voltage Division between two non-zero points**

$$V_{DD} \rightarrow R_1 \rightarrow V_1 \rightarrow R_2 \rightarrow V_{EE} \quad (\text{superposition})$$


$$V_1 = V_{DD} \frac{R_2}{R_1 + R_2} + V_{EE} \frac{R_1}{R_1 + R_2}$$

**AC Resistors and Capacitors**

$$R \parallel \frac{1}{Cs} = \frac{R \frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{R}{RCs + 1}$$

$$\frac{R}{R + \frac{1}{Cs}} = \frac{RCs}{RCs + 1} = \frac{s}{s + \frac{1}{RC}}$$

$$\frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{1}{RCs + 1}$$

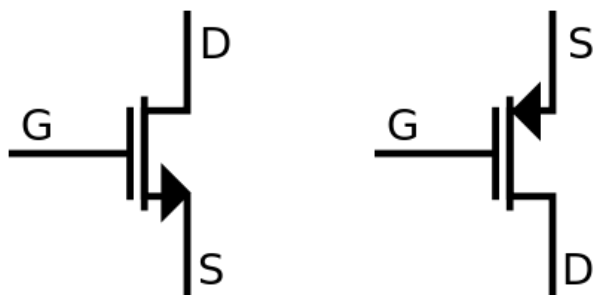**MOS**

NMOS

PMOS

**MOS DC Biasing**


- this is all for NMOS. PMOS is backward
- $\beta = k'_n \left(\frac{W}{L}\right)$
- cutoff:  $V_{GS} < V_{th}$   
\*  $I_D = 0$
- triode (linear):  $V_{DS} < V_{GS} - V_{th}$   
\*  $I_D = k'_n \frac{W}{L} \left( (V_{GS} - V_{th})V_{DS} - \frac{V_{DS}^2}{2} \right)$
- active (saturation):  $V_{DS} > V_{GS} - V_{th}$   
\*  $I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{th})^2$   
\* overdrive voltage  $V_{ov} = V_{GS} - V_{th}$
- to show it's active: show that  $V_{DS} > V_{ov}$  (or  $V_{DS} > V_{GS} - V_{th}$ )

**MOS Small Signal**

	$\frac{V_o}{V_g}$	$R_i$	$R_o$
CS	$-\frac{R_D \parallel R_L}{\frac{1}{g_m} + R_S}$	$R_{G1} \parallel R_{G2}$	$R_D$
CG	$\frac{R_D \parallel R_L}{R_i}$	$\frac{1}{g_m}$	$R_D$
CD	$\frac{R_L}{\frac{1}{g_m} + R_L}$	$R_{G1} \parallel R_{G2}$	$\frac{1}{g_m}$

$$g_m = k' \frac{W}{L} (V_{GS} - V_t) = k' \frac{W}{L} (V_{ov}) = \sqrt{2k' \frac{W}{L} I_D}$$

- CS: Common Source
- CG: Common Gate
- CD: Common Drain (buffer)
- apparently, when calculating the max gain of the frequency response, it is OK to just use the part of the equation that doesn't depend on  $s$

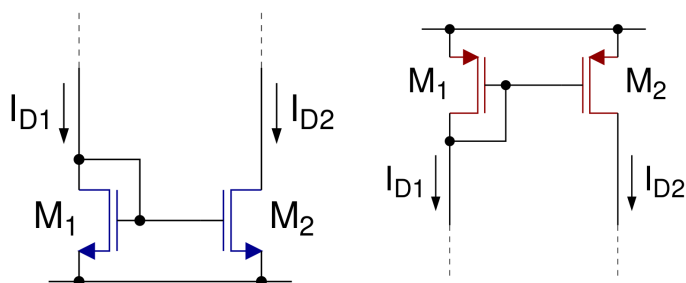**MOS current mirrors**

NMOS

PMOS

- where M1 is the transistor with base shorted to ground (the reference branch)
- $\frac{I_{D1}}{I_{D2}} = \frac{(W/L)_1}{(W/L)_2}$  or  $I_{D2} = \frac{(W/L)_2}{(W/L)_1} I_{D1}$

**Bode Plots**


- magnitude is plotted in dB:  
 $|T(j\omega)|_{dB} = 20 \log_{10} |T(j\omega)|$
- starts on y-axis at DC offset with slope 0
- just add together the bode plots of each individual pole, zero, and the DC offset
- poles always slope down, zeros slope up (applies for both magnitude and phase)
- dec=decade, e.g. from  $10^0$  to  $10^1$
- magnitude:
  - \* Pole/Zero at origin:  
constant slope  $\pm 20\text{dB/dec}$  for all  $\omega$ ;  $0\text{dB}$  at  $\omega = 10^0 = 1$
  - \* Pole/Zero at  $\omega_0$ :  
0 for  $\omega < \omega_0$   
slope  $\pm 20\frac{\text{dB}}{\text{dec}}$  after

- \* Constant  $C$ : constant line at  $20 \log_{10}(|C|)$
- phase:
  - \* Pole at origin: constant  $-\frac{\pi}{2}$  or  $-90^\circ$
  - \* Zero at origin: constant  $+\frac{\pi}{2}$  or  $+90^\circ$
  - \* Pole/Zero at  $\omega_0$ :
    - 0 for  $\omega < \frac{\omega_0}{10}$
    - slope linearly ( $\pm 45^\circ/\text{dec}$ ) until  $10\omega_0$
    - 0 slope for  $\omega > 10\omega_0$
  - \* Constant  $C$ : no effect (0 for all  $\omega$ )
- Prof wants us to actually show the -3dB drop curve, not just a straight intersection
- on the x-axis of the bode plot you need to plot frequency in Hz, so take  $s = j\omega$  and divide by  $2\pi$


### Solving systems with Op Amps

- only applies if the op-amp has feedback
- step 0: if the op amp is ideal, write out ideal properties:
  - \*  $V_+ = V_-$
  - \*  $I_- = 0, I_+ = 0$
  - \*  $A \approx \infty$
- avoid doing KCL/KVL directly on the output node of the op amp
- ignore resistors from a point at 0V to ground

### Op Amp Equations

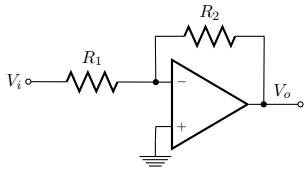

Inverting Amplifier

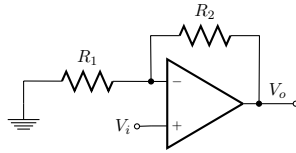


Non-Inverting Amplifier

- ideal open-loop behavior:  $(V_p - V_n) > 0 \rightarrow V_o = V_{DD}$   
 $(V_p - V_n) < 0 \rightarrow V_o = -V_{DD}$
- general form:  $T(s) = \frac{K_0}{1 + \frac{s}{\omega_0}}$ 
  - \*  $T(0) = K_0$ : DC offset. For these simple ones, it's equal to ideal response
  - \*  $\omega_0 = \frac{\omega_t}{1 + R_2/R_1}$
- inverting op amp:
  - \* ideal:  $T(s) = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$
  - \* non-ideal:
 
$$T(s) = \frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \frac{1+R_2/R_1}{A(s)}} = \frac{-R_2/R_1}{1 + \frac{s}{\left(\frac{\omega_t}{1+R_2/R_1}\right)}} = \frac{-R_2/R_1}{1 + \frac{s}{\omega_0}}$$
- non-inverting op-amp:
  - \* ideal:  $T(s) = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$
  - \* non-ideal:
 
$$T(s) = \frac{V_o}{V_i} = \frac{1+R_2/R_1}{1 + \frac{1+R_2/R_1}{A(s)}} = \frac{1+R_2/R_1}{1 + \frac{s}{\left(\frac{\omega_t}{1+R_2/R_1}\right)}} = \frac{1+R_2/R_1}{1 + \frac{s}{\omega_0}}$$

### RC Filter

- Transmission Function:  $T(s) = \frac{V_o(s)}{V_i(s)}$
- Corner frequency: frequency  $s$  at which  $T(s) = \frac{1}{\sqrt{2}}$
- for simple circuit: ground  $\rightarrow$  source  $\rightarrow R \rightarrow C \rightarrow$  ground
  - \*  $T(s) = \frac{1}{1+RCs}$
  - $|T(j\omega)| = \frac{1}{\sqrt{1+R^2C^2s^2}}$
  - $|\angle T(j\omega)| = \frac{1}{\sqrt{1+R^2C^2s^2}}$
- low pass

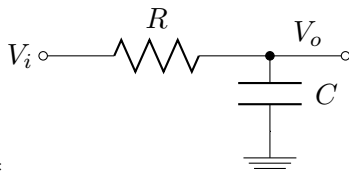


\*  $T(s) = \frac{V_o}{V_i} = \frac{1}{1+RCs}$

\* corner frequency:  $s = \frac{1}{RC}$  (also pole)

\* pole:  $\frac{1}{RC}$

• high pass

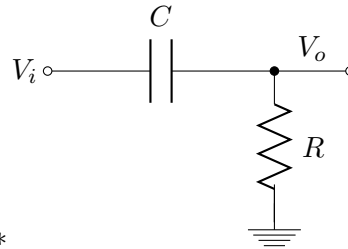

\*  $T(s) = \frac{V_o}{V_i} = \frac{RCs}{1+RCs}$

\* zero:  $s = 0$ , pole:  $s = \frac{1}{RC}$