

# ECEN454 refsheets

<https://github.com/joshua-wright>

## specifically for final

- exam 1 was on March 8 (2017.03.08)
- nothing specifically from previous exam
- HW6 was due on March 8, so exam is HW7-HW11

## Propagation vs Contamination delay

- contamination delay ( $t_{cd}$ ): time from input change to **any** output changing value
  - kind of a best-case delay or smallest possible delay
  - time counted when input crosses 50% of logical high voltage level
- propagation delay: time from when all inputs are stable to when all outputs are stable
  - kind of like a worst-case delay

## static vs dynamic power

- static power
  - consumed when circuit is not active
  - e.g. leakage current
  - static because no inputs are changing
- dynamic power
  - power consumed due to gates switching and stuff
  - e.g. charging/discharging parasitic caps, etc...

## Latch vs Flip Flop

- Latch is level-sensitive, flip-flop is edge-sensitive
- register is flip-flop

## Latch/flip flop designs

- pass transistor latch
  - pros: tiny, low clock load
  - con: voltage drop across is  $V_t$ , it's non-restoring
  - con: not really a latch because doesn't hold signal
- transmission gate
  - pro: no  $V_t$  drop
  - con: requires inverted clock
- inverting buffer
  - TODO

- tristate feedback
  - first complete latch here
  - risk of backdriving: downstream could change state if it is very strong
- buffered output
  - no backdriving problem
  - widely used
  - rather large and slow though, and large load on clock
- a flip-flop is just two latches back-to-back

## Metastability

- stable works if it's not at a strong high or low but will settle somewhere
- metastable is where it might sit there, but if it must settle, you don't know which one it will settle to when perturbed

2017.03.22

## Interconnect

- contacts
  - have resistance  $2 - 20\Omega$
  - so use a bunch of them to reduce resistance between layers
- lumped RC model
  - when you lump together RC sections for speed
  - $\pi$ -model (pi-model) is most commonly used
- distributed RC model: opposite of lumped model
- crosstalk
  - caused by parasitic cap between wires
  - one wire changing voltage can induce noise on adjacent wires and/or increase delay

B	$\Delta V$	$C_{eff}(A)$	MCF
Constant	$V_{DD}$	$C_{gnd} + C_{adj}$	1
With A	0	$C_{gnd}$	0
Opposite A	$2V_{DD}$	$C_{gnd} + 2C_{adj}$	2

- **MCF: Miller Effect:** effect of crosstalk
  - quantifies crosstalk delay
  - use MCF factor to determine effective parasitic capacitance between two signal wires
- Elmore delay: split into segments and use pi-model (or some other model)
  - wire delay is quadratically proportional to length of wire
  - by each C:  $t_{pd} = \sum_{i:=caps} R_{i-to-source} C_i$
  - by each R:  $t_{pd} = \sum_{i:=resistors} R_i C_{downstream}$ 
    - \* downstream capacitors: if the cap is not along the direct path between the source and the point you're interested in, you just ignore that R for some reason (based on HW)
- repeaters/buffers:
  - worth it only if wire is sufficiently long
  - $t_{unbuf} = R(cx + C) + rx(cx/2 + C)$
  - $t_{buf} = 2R(cx/2 + C) + rx(cx/4 + C) + t_b$ 
    - \*  $x$ : wire length
    - \*  $R$ : buffer output resistance
    - \*  $C$ : buffer input capacitance
    - \*  $r$ : wire unit length resistance
    - \*  $c$ : wire unit length capacitance

- \*  $t_b$ : buffer delay time
- time difference:  $\Delta t = t_{buf} - t_{unbuf} = RC + t_b - rcx^2/4$
- buffers help slack because they decouple parasitic capacitance

2017.03.27

## Sequential Circuits

- sequential means that the circuit holds state: the output depends on both current and past input
- to model a state machine, you can unroll it to [register]  $\rightarrow$  [combinational]  $\rightarrow \dots$ 
  - this way you can use regular timing stuff for it: arrival time, slack, etc...
- Mealy FSM: output of circuit is from combinational logic
- Moore FSM: output is from registers
- pipelined circuit: uses registers to hold state between clock cycles, because not all of the combinational logic can happen fast enough to work in a single clock cycle
  - pipelined circuits can use flip-flops or latches?
- the clock consumes 20-30% of the power on a chip
- the whole reason that registers are needed is because data (signals) moves through components at non-constant speed
- reset
  - can be sync or async
  - force low output when reset is high
- sequencing: it is (generally) equivalent to split the sequential logic in two, and then use two latches (one halfway through) instead of one large section of sequential logic with flip-flops at either end
  - this is called two phase clocking
  - you have to make sure the middle latch operates on clock-bar instead of clock

symbol	definition
$t_{pd}$	logic propagation delay
$t_{cd}$	logic contamination delay
$t_{pcq}$	Clk $\rightarrow$ Q propagation delay
$t_{ccq}$	Clk $\rightarrow$ Q contamination delay
$t_{pdq}$	D $\rightarrow$ Q propagation delay
$t_{setup}$	setup time of flip-flop/latch
$t_{hold}$	hold time of flip-flop/latch

- timing:
  - D $\rightarrow$ Q delay only makes sense for latches, since for flip-flops it is simply one clock cycle
- sequencing overhead and max delay:
  - $T_c$ : cycle time
  - need for combinational logic to be fast enough
  - for single phase flip flop:  $t_{pd} < T_c - (T_{setup} + T_{pcq})$
  - for two-phase latch:  $t_{pd} = t_{pd1} + t_{pd2} < T_c - 2t_{pdq}$
  - max delay is dictated by cycle time and sequencing overhead; sequencing overhead does not effect minimum delay
- minimum delay:
  - for single phase flip flop:  $t_{cd} > t_{hold} - t_{ccq}$ 
    - \* combinational stuff must be slow enough that it doesn't violate hold time of second flip flop
  - for two-phase latch:  $t_{cd1}, t_{cd2} > t_{hold} - t_{ccq} - t_{non-overlap}$ 
    - \* hold time applies twice each cycle, once per each combinational circuit
    - \*  $t_{non-overlap}$ : phase between clock signals
- time borrowing: for two-phase latch-based system, you can borrow time from one segment to the other while the latch is transparent
  - works (is possible) as long as the total circuit still completes within one clock cycle

- will need to change the phase the phase of the second clock
- clock skew:
  - when uncertain: causes tighter required CL propagation delay and minimum CL contamination delay, and reduces opportunity for time borrowing.
  - when know constant skew: can help with same effect as time borrowing, except it can also work for flip-flop based systems
- skew tolerance:
  - flip-flop circuits are not very skew tolerant because the setup and hold times define a specific window of time in which the data must arrive
  - latch circuits are more hold-time-tolerant because the data can arrive any time that the latch is transparent
- if setup times are violated, you can reduce clock speed to fix it
- if hold times are violated, it won't work at any clock speed

2017.03.29

## Clocking

- H-Tree (clock distribution network)
  - laid out in such a way that the delay from the center to any leaf node is equal
  - if you're missing one of the nodes, just don't draw that part. Make sure the rest of the H-tree is the exact same shape though, so that the distances are the same
- Grid clock distribution
  - grid on two or more levels
  - ensures low local skew, but there could still be larger chip-wide skew
- generally, the longer the delay between two point, the larger the worst-case clock skew
- Domino circuit: TODO
  - a kind of dynamic logic
  - when the clock pulse cascades through the circuit, activating the pMOS at each stage?

2017.04.03 (+more)

## Memory

- random access or sequential access, or content addressable
- CAM: content-addressable memory
  - basically like an associative array, or database
  - designed to search all memory at once in a single operation (wikipedia)
  - used in caches
- SRAM:
  - 12T and 6T cell designs
  - 12T design: just a latch connected to a bitline
    - \* boring and impractical because it's too large
  - 6T design: cross-coupled inverters (3T each) +2T for bit and bit-bar lines
    - \* we focus on 6T design
  - read: pre-charge bit and bit-bar, raise wordline, read result
    - \* need to pre-charge both bit and bit-bar to 1 or else read is destructive
    - \* need sense amplifiers at the end of the bitlines because the signal will be weak
    - \* the parasitic capacitance of the bitline depends on how many cells are 0 or 1
  - write: drive data onto bit and bit-bar and raise wordline to write
  - cross coupled inverters must be much larger than the bitline transistors so that it doesn't flip while reading
  - per each column, you need:
    - \* piece of decoder
    - \* bitline sense amplifier
    - \* column multiplexer

- multi-port: means you can read from and write to the same cell in the same clock cycle and it works
  - \* implement by having multiple sequential read/write per cycle?
- decoders:
  - must be pitch-matched to SRAM cell width for layout efficiency/simplicity (requires very skinny gates)
  - large ( $n > 4$ ) decoders are inefficient, thus it is often helpful to use predecoding: factor out common gates into a second stage of decoders.
    - \* smaller area as alternative, but same logical effort (since same number of gates traversed)
- twisted bitlines: bitlines are long and right next to each other, so there will be significant crosstalk and parasitic cap
  - solution: swap adjacent bit and bit-bar lines occasionally
  - reduces Miller factor (MCF)
- DRAM:
  - one transistor and one capacitor
    - \* transistor gates capacitor
  - no charge is 0, charge is 1
  - open transistor to read/write
  - read is destructive
  - must be refreshed periodically due to leakage
    - \* thus, it's always consuming power
- shift register:
  - can be implemented with cascade of flip-flops
    - \* can lead to hold time violations because no delay from clock to next data line
      - problems when the  $\text{Clk} \rightarrow \text{Q}$  time is less than the hold time of the flip-flop
    - \* not very dense
  - store data in SRAM and store begin/end pointers
    - \* more dense than individual flip-flops
- Tapped Delay Line
  - shift register with programmable number of stages
  - implement using sequence of flip-flops, each with a bypass MUX from data in to out
- Queues: are a thing (TODO)
- ROM: Read Only Memory:
  - mask-programmed ROMs are one transistor per bit
- PROMs, EPROMs, etc
  - generally burn out specific fuses to program ROM
  - E for erasable

2017.04.10, 2017.04.12

## Low Power Design

- not so useful when running from a battery since batteries store energy, not power
  - doing the same computation slower will use the same energy from the battery (generally)
- peak power
  - determines power/ground wiring and packaging limits
  - impacts signal/noise ratio
- reduce dynamic power: (AKA active power)
  - use smaller transistors
  - clock gating
  - reduce  $V_{DD}$
  - reduce frequency
    - \* but be careful because that will make the computations take longer
- reduce static power
  - power gating
  - selectively use lower  $V_{DD}$  devices
  - stacked devices

- body bias
- clock gating: disable the clock signal to an expensive component
  - eliminates that component's dynamic power (but of course you can't use it)
  - doesn't change static power
- voltage islands: different  $V_{DD}$  for different devices
  - allow low  $V_{DD}$  devices to run slower because they don't need to be fast (maybe they're not in the critical path)
  - often different voltage levels are alternated row by row in standard-cell layouts
  - you must convert from one logic level to another, because high/low will be different
    - \* sometimes it's possible to avoid conversion, e.g. by using a buffer that you would have anyway, with inverters built from half high- $V_{DD}$  transistors and half low- $V_{DD}$  transistors
  - there are all kinds of tricks for determining which components should be high/low voltage and where to put voltage islands and level converters
- DFVS: Dynamic Frequency and Voltage Scaling
  - requires:
    - \* programmable clock generator (PLL)
    - \* supply regulation loop to for setting minimum  $V_{DD}$
    - \* software support for deciding best stable frequency and voltage for given load and performance goals
  - voltage regulation loop (charge pump)
    - \* voltage divider would be horribly inefficient
    - \* instead, rapidly charge/discharge capacitor
- stacked devices:
  - stacking devices reduces leakage
  - because leakage is exponentially proportional to  $V_{ds}$
- body bias AKA dual  $V_t$ 
  - changing  $V_t$  at runtime is called Adaptive Body-Biasing (ABB) or Dynamic Threshold Scaling (DTS)
    - \* requires triple well fabrication process, because what would have been lowest level substrate must itself sit inside a well that will be biased
  - design with low and high  $V_t$
  - low  $V_t$  is faster than high  $V_t$  but consumes 10x more power
    - \* because reducing  $V_t$  increases sub-threshold leakage exponentially
    - \* but reducing  $V_t$  decreases gate delay (increasing performance)
  - to increase  $V_t$ , put a negative bias on  $V_{SB}$  of nMOS
    - \* use DC charge pump to get desired voltage
- power gating: use sleep transistors
  - basically cut off  $V_{DD}$  from power-hungry circuits when not in use
  - in sleep mode, the sleeping transistors are stacked with the transistors that are causing them to sleep, thus reducing leakage even more
- MTCMOS sleep transistors
  - combines power gating and dual  $V_t$
  - TODO what is this?

2017.04.17

## Packaging

- provides:
  - heat dispersion
  - mechanical stability
  - prevent thermal expansion
  - IO
- SMD: Surface Mount Device
- SMT: Surface Mount Technology
- package types
  - DIP: Dual In-line Package

- QFP: Quad Flat Package
- PLCC: Plastic leaded chip Carrier
- BGA: Ball Grid Array
- PGA: Pin Grid Array
- MCM: Multi Chip Module
- DIP: Dual In-line Package
  - basic chip with two sides and pins pointing either down (through hole) or out to the sides (surface mount)
- QFP: Quad Flat Package
  - looks about the same as DIP with SMD pins but has pins pointing out of all 4 sides
- PLCC: Plastic leaded chip Carrier
  - like QFP but instead of pins has tiny pads (J-leads) on perimeter of chip.
  - can sit in a socket with spring connectors that contact those pads
- BGA: Ball Grid Array
  - can have lots of pins
  - can attach to substrate with flip chip or wires
  - underside has pads for where solder balls go to connect to board
- PGA: Pin Grid Array
  - like BGA but with pins
- MCM: Multi Chip Module
  - when you put multiple dies on a single chip
  - advantage over very large single die: you can then select just the working ones of each die component
  - disadvantage: means you'll probably want to test chips before you package them
- flip-chip
  - also called C4: Controlled Collapse Chip Connection
  - just flip the chip over, thus placing the connecting pads on the highest metal layer
  - affix chip to package using a BGA-style connection
  - advantages
    - \* higher pin density
    - \* can put pins anywhere without worrying about routing
- package parasitics
  - parasitics inductance isn't really a problem inside the chip, but is for connecting wires in packaging
- heat dissipation
  - formula:  $\Delta T = \theta_{ja} P$ 
    - \*  $\Delta T$ : change in temperature on chip
    - \*  $\theta_{ja}$ : thermal resistance of chip junction to ambient
    - \*  $P$ : power dissipation on chip
    - \*  $\theta$  adds in series for chip→package and package→headsink
  - must cool chip to avoid things like thermal resistance and electro-migration
  - thermal resistance can cause the chip to fail, but that's only temporary
    - \* should work again after cooling
  - electro-migration: electrons moving where they shouldn't inside the chip
    - \* permanent build-up of problem
- power distribution
  - want to minimize power noise
  - voltage will drop due to
    - \*  $IR$  drop
    - \*  $L * (di/dt)$  noise (from parasitics inductance)
  - decoupling capacitors
    - \* aka bypass caps
    - \* cap between  $V_{DD}$  and ground to smooth out voltage supply
    - \* use multiple caps in series to avoid problems with the resonant frequency of any single cap
- I/O
  - must protect against ESD
  - pad types:
    - \*  $V_{DD}/GND$
    - \* output
    - \* input

- \* bidirectional
  - \* analog
- latch-up
  - \* when noise or density or something causes transistors to do weird things or something
  - \* TODO
- output
  - \* need to drive relatively large off-chip loads, so usually require chain of successively larger buffers
  - \* protect against latch-up using guard ring: p+ inner ring and n+ outer ring (in n-well)
- input
  - \* must do level conversion
  - \* must filter noise
    - use Schmitt trigger: basically doesn't cross threshold unless extra oomph provided (it's sticky)
- bidirectional
  - \* combined input/output pad
  - \* chip has enable signal to decide direction
- analog
  - \* must avoid distorting or delaying the signal at all (no buffering)
  - \* ESD protection circuit must not distort the signal
- ESD protection: TODO
  - ESD: Electro-Static Discharge
  - can damage circuits with too much current and voltage
  - limit current using resistor in series
  - limit voltage using two diodes:
    - \* one from ground to signal line (pointing toward signal line),
    - \* one from signal line to  $V_{DD}$  (pointing toward  $V_{DD}$ )
- MOSIS IO pads
  - library of IO pad designs
  - provides IO protection and stuff

2017.04.26

## Testing

- logic verification is very important
  - consumes 50% of total IC development time
- 3 types:
  - LV: Logic Verification
  - SD: Silicon Debug
  - MT: Manufacturing Test
- LV: Logic Verification
  - simulate chip and see if implementation is correct (does what expected)
  - when you can't test every possible combination (because too many bits and/or too much state), test edge cases
- SD: Silicon Debug
  - test fabricated chips
  - check for logic failures and electrical failures
  - logic: bad implementation
  - electrical: crosstalk, leakage, charge sharing, etc...
  - fixing bugs requires redesigning and re-fabricating the chip
- MT: Manufacturing Test
  - check that the chip was fabricated without error
    - \* e.g. no speck of dust came in and killed the chip
  - yield is always <100% because fabrication is never perfect
  - testing machines are super expensive so you gotta balance number of test cases (test coverage) vs cost
- Smoo Plot



- used to diagnose chip failures
  - 2D plot of frequency vs  $V_{DD}$
  - X or not depending if chip passed test at that frequency and supply voltage
  - can help to tell what is causing failures
- stuck-at fault
  - model a failure as stuck at 0 or 1
  - there’s a whole bunch of ways that silicon could be manufactured incorrectly, but stuck-at fault models most of these approximately right
- observability: how easy it is to observe a node at the output
  - to observe a node at the output, the output must be determined by that node
- controllability: how easy it is to force a node to a specific value
- combinational logic has good observability and controllability, finite state machines (FSMs) do not
- test pattern generation:
  - apply smallest possible sequence of test vectors necessary to show that each node is not stuck
  - circuits with better controllability and observability are more testable (can be fully tested with fewer test patterns)
- scan register, scan chain
  - add a mux to the input of all registers, linking them together in a big optional shift register
  - then you can shift pre-defined values into all registers for testing, and shift out the test results
  - makes the circuit more testable
- ATPG: Automatic Test Pattern Generation
  - given blocks of combinational logic, generates test patterns for use with scan chains
- built in self test
  - circuits that test themselves using built-in test pattern generators and verifiers
- PRSG: Pseudo-Random Sequence Generator
  - just a linear feedback shift register with input as XOR of state
  - used for random testing
- BILBO: Built-in Logic Block Observer
  - automatic tester
- boundary scan
  - basically a scan chain for all the pins (boundaries)
  - because some packaging types (e.g. BGA) are hard to make temporary sockets for