

ECEN454 refsheets

<https://github.com/joshua-wright>

specifically for final

- exam 1 was on March 8 (2017.03.08)
- nothing specifically from previous exam

Propagation vs Contamination delay

- contamination delay (t_{cd}): time from input change to **any** output changing value
- kind of a best-case delay or smallest possible delay
- time counted when input crosses 50% of logical high voltage level
- propagation delay: time from when all inputs are stable to when all outputs are stable
- kind of like a worst-case delay

Latch vs Flip Flop

- Latch is level-sensitive, flip-flop is edge-sensitive
- register is flip-flop # Latch/flip flop designs
- pass transistor latch
 - pros: tiny, low clock load
 - con: voltage drop across is V_t , it's non-restoring
 - con: not really a latch because doesn't hold signal
- transmission gate
 - pro: no V_t drop
 - con: requires inverted clock
- inverting buffer
 - TODO
- tristate feedback
 - first complete latch here
 - risk of backdriving: downstream could change state if it is very strong
- buffered output
 - no backdriving problem
 - widely used
 - rather large and slow though, and large load on clock
- a flip-flop is just two latches back-to-back

Metastability

- stable works if it's not at a strong high or low but will settle somewhere
- metastable is where it might sit there, but if it must settle, you don't know which one it will settle to when perturbed

Sequential Circuits

- sequential means that the circuit holds state: the output depends on both current and past input
- to model a state machine, you can unroll it to [register] \rightarrow [combinational] $\rightarrow \dots$
 - this way you can use regular timing stuff for it: arrival time, slack, etc...
- Mealy FSM: output of circuit is from combinational logic
- Moore FSM: output is from registers
- pipelined circuit: uses registers to hold state between clock cycles, because not all of the combinational logic can happen fast enough to work in a single clock cycle
 - pipelined circuits can use flip-flops or latches?
- the clock consumes 20-30% of the power on a chip
- the whole reason that registers are needed is because data (signals) moves through components at non-constant speed
- reset
 - can be sync or async
 - force low output when reset is high
- sequencing: it is (generally) equivalent to split the sequential logic in two, and then use two latches (one halfway through) instead of one large section of sequential logic with flip-flops at either end
 - this is called two phase clocking
 - you have to make sure the middle latch operates on clock-bar instead of clock
- timing:
 - t_{pd} logic propagation delay
 - t_{cd} logic contamination delay
 - t_{pcq} Clk \rightarrow Q propagation delay
 - t_{ccq} Clk \rightarrow Q contamination delay
 - t_{pdq} D \rightarrow Q propagation delay
 - t_{setup} setup time of flip-flop/latch
 - t_{hold} hold time of flip-flop/latch
 - D \rightarrow Q delay only makes sense for latches, since for flip-flops it is simply one clock cycle
- sequencing overhead and max delay:
 - T_c : cycle time
 - need for combinational logic to be fast enough
 - for single phase flip flop: $t_{pd} < T_c - (T_{setup} + T_{pcq})$
 - for two-phase latch: $t_{pd} = t_{pd1} + t_{pd2} < T_c - 2t_{pdq}$
 - max delay is dictated by cycle time and sequencing overhead; sequencing overhead does not effect minimum delay
- minimum delay:
 - for single phase flip flop: $t_{cd} > t_{hold} - t_{ccq}$
 - * combinational stuff must be slow enough that it doesn't violate hold time of second flip flop
 - for two-phase latch: $t_{cd1}, t_{cd2} > t_{hold} - t_{ccq} - t_{non-overlap}$
 - * hold time applies twice each cycle, once per each combinational circuit
 - * $t_{non-overlap}$: phase between clock signals?
- time borrowing: for two-phase latch-based system, you can borrow time from one segment to the other while the latch is transparent
 - works (is possible) as long as the total circuit still completes within one clock cycle
- clock skew:
 - when uncertain: causes tighter required CL propagation delay and minimum CL contamination delay, and reduces opportunity for time borrowing.
 - when know constant skew: can help with same effect as time borrowing, except can also have effect for flip-flop based systems
- skew tolerance:
 - flip-flop circuits are not very skew tolerant because the setup and hold times define a specific window of time in which the data must arrive
 - latch circuits are more hold-time-tolerant because the data can arrive any time that the latch is transparent

- if setup times are violated, you can reduce clock speed to fix it
- if hold times are violated, it won't work at any clock speed

2017.03.29

Clocking

- H-Tree (clock distribution network)
 - laid out in such a way that the delay from the center to any leaf node is equal
- Grid clock distribution
 - grid on two or more levels
 - ensures low local skew, but there could still be larger chip-wide skew
- generally, the longer the delay between two point, the larger the worst-case clock skew
- Domino circuit: TODO
 - a kind of dynamic logic
 - when the clock pulse cascades through the circuit, activating the pMOS at each stage?

2017.04.03 (+more)

Memory

- random access or sequential access, or content addressable
- CAM: content-addressable memory
 - basically like an associative array, or database
 - designed to search all memory at once in a single operation (wikipedia)
 - used in caches
- SRAM: TODO
 - 12T and 6T cell designs
 - 12T design: just a latch connected to a bitline
 - * boring and impractical because it's too large
 - 6T design: cross-coupled inverters (3T each) + 2T for bit and bit-bar lines
 - * we focus on 6T design
 - read: pre-charge bit and bit-bar, raise wordline, read result
 - * (need to pre-charge or else read is destructive?)
 - * need sense amplifiers at the end of the bitlines because the signal will be weak, and the parasitic capacitance of the bitline depends on how many cells are 0 or 1
 - write: drive data onto bit and bit-bar and raise wordline to write
 - cross coupled inverters must be much larger than the bitline transistors so that it doesn't flip while reading
 - per each column, you need:
 - * piece of decoder
 - * bitline sense amplifier
 - * column multiplexer
 - multi-port: means you can read from and write to the same cell in the same clock cycle and it works
 - * implement by having multiple sequential read/write per cycle?
- decoders:
 - must be pitch-matched to SRAM cell width for layout efficiency/simplicity (requires very skinny gates)
 - large ($n > 4$) decoders are inefficient, thus it is often helpful to use predecoding: factor out common gates into a second stage of decoders.
 - * smaller area as alternative, but same logical effort (since same number of gates traversed)
- twisted bitlines: bitlines are long and right next to each other, so there will be significant crosstalk and parasitic cap
 - solution: swap adjacent bit and bit-bar lines occasionally
 - reduces Miller factor (MCF)
- DRAM: TODO

- one transistor and one capacitor
 - * transistor gates capacitor
 - no charge is 0, charge is 1
 - open transistor to read/write
 - read is destructive
 - must be refreshed periodically due to leakage
 - * thus, it's always consuming power
- shift register:
 - can be implemented with cascade of flip-flops
 - * can lead to hold time violations because no delay from clock to next data line? (TODO what? how?)
 - * not very dense
 - store data in SRAM and store begin/end pointers
 - * more dense than individual flip-flops
- Tapped Delay Line
 - shift register with programmable number of stages
 - implement using sequence of flip-flops, each with a bypass MUX from data in to out
- Queues: are a thing (TODO)
- ROM: Read Only Memory:
 - mask-programmed ROMs are one transistor per bit
- PROMs, EPROMs, etc
 - generally burn out specific fuses to program ROM
 - E for erasable

2017.04.10

Low Power Design

- not so important when running from a battery since batteries store energy, not power
- peak power
 - determines power/ground wiring and packaging limits
 - impacts signal/noise ratio