

Metric Prefixes

peta	P	10^{15}	1 000 000 000 000 000
tera	T	10^{12}	1 000 000 000 000
giga	G	10^9	1 000 000 000
mega	M	10^6	1 000 000
kilo	k	10^3	1 000
hecto	h	10^2	100
deca	da	10^1	10
one		10^0	1
deci	d	10^{-1}	0.1
centi	c	10^{-2}	0.01
milli	m	10^{-3}	0.001
micro	μ	10^{-6}	0.000 001
nano	n	10^{-9}	0.000 000 001
pico	p	10^{-12}	0.000 000 000 001
femto	f	10^{-15}	0.000 000 000 000 001

RC Filter

- Transmission Function: $T(s) = \frac{V_o(s)}{V_i(s)}$
- Corner frequency: frequency s at which $T(s) = \frac{1}{\sqrt{2}}$
- for simple circuit: ground \rightarrow source $\rightarrow R \rightarrow C \rightarrow$ ground
 - * $T(s) = \frac{1}{1+RCs}$
 - $|T(j\omega)| = \frac{1}{\sqrt{1+R^2C^2s^2}}$
 - $|\angle T(j\omega)| = \frac{1}{\sqrt{1+R^2C^2s^2}}$

Bode Plots

- magnitude is plotted in dB :
 - $|T(j\omega)|_{dB} = 20 \log_{10} |T(j\omega)|$
- starts on y-axis at DC offset with slope 0
- just add together the bode plots of each individual pole, zero, and the DC offset
- poles always slope down, zeros slope up (applies for both magnitude and phase)
- dec =decade, e.g. from 10^0 to 10^1
- magnitude:
 - * Pole/Zero at origin:
 - constant slope $\pm 20db/dec$ for all ω ; $0dB$ at $\omega = 10^0 = 1$
 - * Pole/Zero at ω_0 :
 - 0 for $\omega < \omega_0$
 - slope $\pm 20 \frac{db}{dec}$ after
 - * Constant C : constant line at $20 \log_{10}(|C|)$
- phase:
 - * Pole at origin: constant $-\frac{\pi}{2}$ or -90°
 - * Zero at origin: constant $+\frac{\pi}{2}$ or $+90^\circ$
 - * Pole/Zero at ω_0 :
 - 0 for $\omega < \frac{\omega_0}{10}$
 - slope linearly ($\pm 45^\circ/dec$) until $10\omega_0$
 - 0 slope for $\omega > 10\omega_0$
 - * Constant C : no effect (0 for all ω)

Solving systems with Op Amps

- step 0: if the op amp is ideal, write out ideal properties:
 - * $V_+ = V_-$
 - * $I_- = 0, I_+ = 0$
- avoid doing KCL/KVL on the output node of the op amp
- ignore resistors from a point at $0V$ to ground